

## E1.4 SOLUTIONS

### Question 1

a) The 10 k $\Omega$  resistor carries the emitter current, so for a collector voltage of 2.5 V we require  $I_E = 0.25$  mA, implying a base current of  $I_B = 250/201 = 1.244$   $\mu$ A. Assuming  $V_{BE} = 0.7$  V, the required value of  $R_B$  is given by  $R_B = (5 - 0.7)/I_B = 3.46$  M $\Omega$ . [6]

b) From the simplified Ebers-Moll equation, the collector currents can be expressed as:

$$I_{C1} = I_S \exp[(V_{IN1} - V_E)/V_T] ; I_{C2} = I_S \exp[(V_{IN2} - V_E)/V_T]$$

where  $V_E$  is the common emitter voltage,  $V_T$  is the thermal voltage, and  $I_S$  is the saturation current (NB assuming identical transistors). It follows that  $I_{C1}/I_{C2} = \exp(V_D/V_T)$ , and we also know that  $I_{C1} + I_{C2} = I$  where  $I$  is the tail current. Eliminating  $I_{C1}$  or  $I_{C2}$  the collector currents are obtained as:

$$I_{C1} = I/[1 + \exp(-V_D/V_T)] ; I_{C2} = I/[1 + \exp(V_D/V_T)]$$

The differential output voltage is then:

$$V_{OUT} = R_C(I_{C1} - I_{C2}) = R_C I \left[ \frac{1}{1 + \exp(-V_D/V_T)} - \frac{1}{1 + \exp(V_D/V_T)} \right] = R_C I \tanh(V_D/2V_T)$$

with  $R_C = 5$  k $\Omega$ ,  $I = 1$  mA, and  $V_T = 25$  mV, the output voltage becomes  $5 \tanh(20V_D)$  as required. [6]

The double-ended differential gain can be obtained simply as the derivative of the large-signal relationship at  $V_D = 0$ :

$$A = \left. \frac{dV_{OUT}}{dV_D} \right|_{V_D=0} = 100 \operatorname{sech}^2(20V_D) \Big|_{V_D=0} = +100$$

A solution based on analysis of the SSEC is also acceptable. [4]

c) Since the transistors are matched, only the finite beta and the output resistance will contribute to the current error. Taking both of these contributions into account, the output current  $I$  can be expressed as:

$$I \approx I_{ref} - 2I/\beta + \Delta V_{CE}/r_o$$

where  $I_{ref}$  is the input current. So, the currents will be equal when  $\Delta V_{CE} \approx 2I r_o/\beta = 2V_A/\beta$ , where we have used  $r_o = V_A/I$ . Putting  $V_A = 120$  V,  $\beta = 100$  gives  $\Delta V_{CE} \approx 2.4$  V, and since the input side transistor has  $V_{CE} = 0.7$  V (assumption), this implies  $V_{OUT} \approx 3.1$  V. [6]

d) Since we are calculating for the case where the MOSFET is at pinch-off, we know we can use the active mode drain current equation. With  $V_G = 0$ , and  $V_S = I_D R_S$ , we need to solve:

$$I_D = V_S/R_S = K(-V_S - V_t)^2 \Rightarrow 2V_S^2 - 5V_S + 2 = 0$$

The roots are  $V_S = 0.5$ ,  $V_S = 2$ , and the valid root is the first one (since second leaves MOSFET sub-threshold). The drain current is  $V_S/R_S = 50 \mu\text{A}$ .

Since  $V_S = 0.5$ , and  $V_{DS} = V_{GS} - V_t = 0.5 \text{ V}$ , the drain voltage is 1.0 V, and the supply voltage is  $V_{DD} = V_D + I_D R_D = 1 + 0.05\text{m} \times 30\text{k} = 2.5 \text{ V}$ .


[6]

e) Before the input pulse, the transistor is off and the circuit is in steady-state with  $I_L = 0$  and  $V_{OUT} = 5 \text{ V}$ . During the input pulse, the base current is  $I_B = (5 - 0.7)/5\text{k} = 0.86 \text{ mA}$ , and the collector current is  $\beta I_B = 172 \text{ mA}$  if transistor is active, or  $< 172 \text{ mA}$  if it is saturated. We have assumed  $V_{BE} = 0.7 \text{ V}$ .

The inductor current is continuous, and the maximum current in the  $100 \Omega$  resistor is  $\approx 50 \text{ mA}$ , so the transistor is initially saturated with  $V_{CE} = V_{CEsat} \approx 0.2 \text{ V}$  (assumption) and  $I_C \approx 48 \text{ mA}$ . With 4.8 V across the inductor, the inductor current will rise at a rate of  $dI_L/dt = V_L/L = 480 \text{ A/sec}$ . By the end of the pulse it will have reached  $480 \times 200\mu = 96 \text{ mA}$ . Since the total load current at this point ( $96 + 48 = 144 \text{ mA}$ ) is  $< 172 \text{ mA}$  we know the transistor does not come out of saturation.


When the transistor switches off, the inductor current will continue to flow in the  $100 \Omega$  resistor, and the output voltage will rise suddenly to  $V_{CC} + I_L R = 5 + 0.096 \times 100 = 14.6 \text{ V}$ . It will then decay exponentially over time, with an asymptotic value of 5 V. The time-constant for this decay will be  $L/R = 0.01/100 = 100 \mu\text{s}$ .

[4]

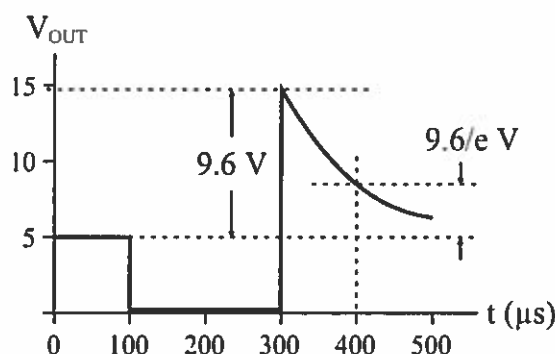

[4]

f)

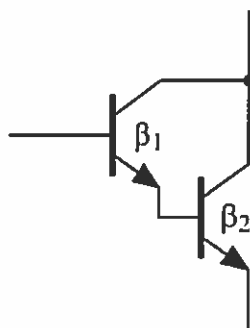

The base current of the RH transistor is  $I_{B2} = (1 + \beta_1)I_{B1}$ . The total collector current for the Darlington pair is  $I_C = I_{C1} + I_{C2} = \beta_1 I_{B1} + \beta_2 I_{B2} = [\beta_1 + (1 + \beta_1)\beta_2]I_{B1}$ . The overall current gain is then  $I_C/I_{B1} = \beta_1 + \beta_2 + \beta_1\beta_2$ .

[4]

## Question 2


a) The drain current will be set by the depletion load which has  $V_{GS} = 0$ . Assuming this device is active (as question suggests), we have  $I_D = K_2(-V_{t2})^2 = 0.45 \text{ mA}$ . The lower MOSFET must be carrying the same current, so we also have  $I_D = K_1(V_{GS1} - V_{t1})^2$ . Rearranging this we obtain  $V_{GS1} = \sqrt{I_D/K_1} + V_{t1} = 1.75 \text{ V}$ , where we have taken the +ve square root because Q1 is above threshold. The potential divider forces  $V_{OUT} = 3V_{GS1}$ , so  $V_{OUT} = 5.25 \text{ V}$ . [6]

Q1 has  $V_{DS} = 5.25 \text{ V}$ ,  $V_{GS} = 1.75 \text{ V}$ ,  $V_t = 1 \text{ V}$ , so  $V_{DS} > V_{GS} - V_t$  and **active**.

Q2 has  $V_{DS} = 10 - 5.25 = 4.75 \text{ V}$ ,  $V_{GS} = 0$ ,  $V_t = -1.5 \text{ V}$ , so also **active**.

Q2 will enter triode when  $V_{DS} = -V_t = 1.5 \text{ V}$ , i.e. when  $V_{DD} = 5.25 + 1.5 = 6.75 \text{ V}$ . [3]

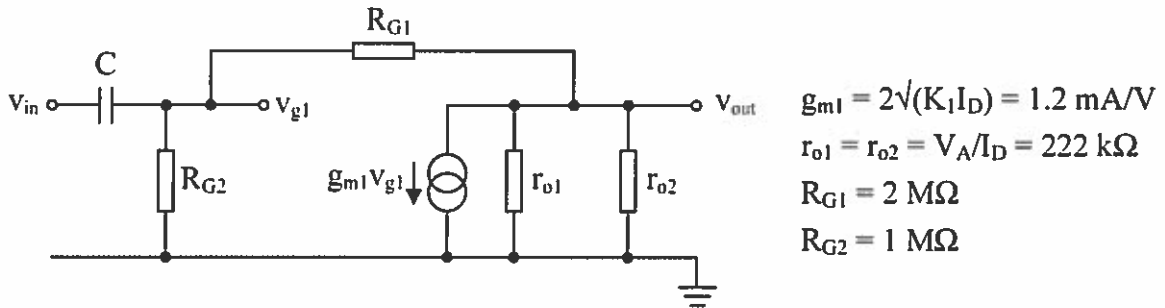b) SSEC (input capacitor may be omitted):




KCL at output gives:  $g_{m1}v_{g1} + v_{out}/r_{o1} + v_{out}/r_{o2} + (v_{out} - v_{g1})/R_{G1} = 0$ . Collecting terms in  $v_{out}$  and  $v_{g1}$ , and noting the  $v_{g1} \approx v_{in}$  in the mid-band, the mid-band gain is obtained as: [6]

$$A_v = v_{out}/v_{g1} = -(g_{m1} - 1/R_{G1}) \cdot (r_{o1} // r_{o2} // R_{G1}) = -1.2 \text{ m} \times 105.3 \text{ k} = -126.3$$
 [3]


The input resistance is  $R_i = R_{G2} // [R_{G1}/(1 - A_v)] = 1 \text{ M} // 15.7 \text{ k} = 15.5 \text{ k}$ . The cut-off frequency of the input filter is  $f_{ci} = 1/(2\pi R_i C)$ , so for  $f_{ci} = 100 \text{ Hz}$  we require  $C = 1/(2\pi R_i f_{ci}) = 103 \text{ nF}$ . [5]

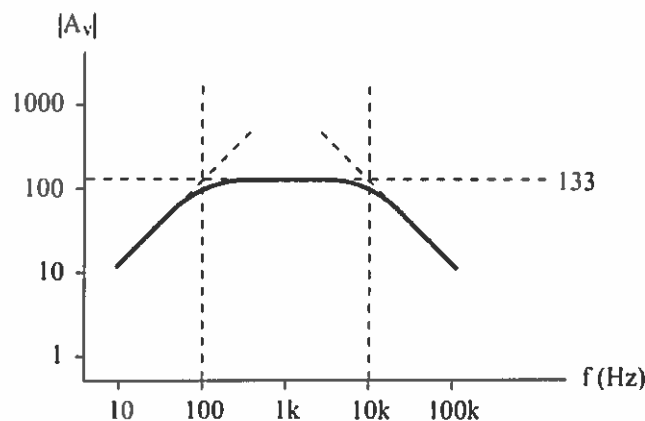c) The load produces a low-pass response, with cut-off  $f_{co} = 1/(2\pi R_o C_L)$  where  $R_o$  is the amplifier output resistance and  $C_L$  is the load capacitance. With  $R_o = r_{o1} // r_{o2} // R_{G1} = 105.3 \text{ k}\Omega$ , and  $C_L = 150 \text{ pF}$ , the cut-off is at  $f_{co} = 10.08 \text{ kHz}$ . [2]



### Question 3

a)

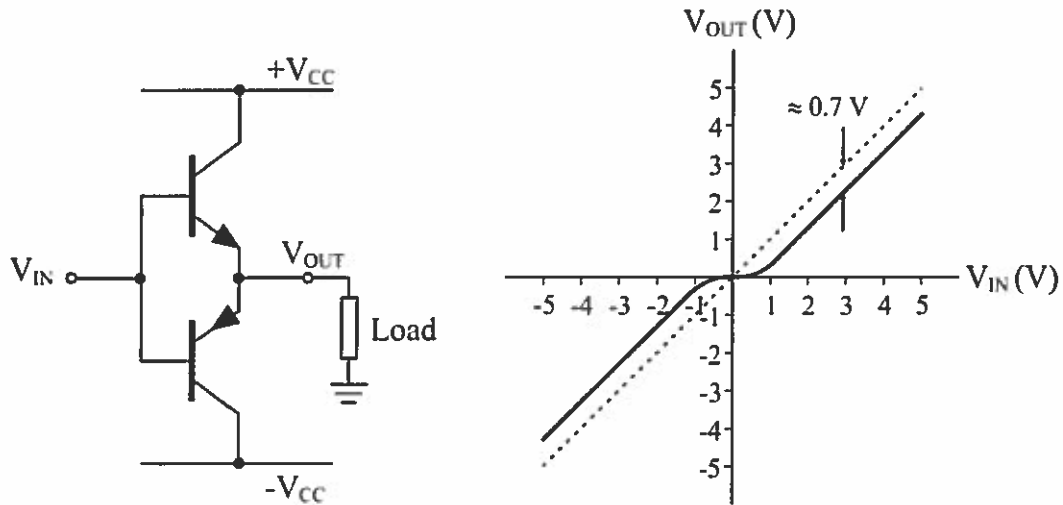

[4 + 4]

The output stage is a unity (voltage) gain amplifier, but there is a  $V_{BE}$  offset between input and output, and a region near the origin where it is unresponsive, leading to cross-over distortion.

[2]

b) From symmetry,  $V_{out} = 0$  occurs when  $V_{in} = 0$ . KVL under these conditions gives:

$$V_{BE1} = V_{BE2} + I_2 R$$

where we have ignored the base current of Q2. From the simplified Ebers-Moll equation we know that  $V_{BE1} = V_T \ln(I_1/I_{S1})$  and  $V_{BE2} = V_T \ln(I_2/I_{S2}) = V_T \ln[I_2/(NI_{S1})]$ . Substituting for  $V_{BE1}$  and  $V_{BE2}$  in the top equation we obtain  $V_T \ln(I_1/I_{S1}) = V_T \ln[I_2/(NI_{S1})] + I_2 R$ . Taking the inverse log of both sides gives the desired result.

[8]

Rearranging the given equation:  $R = (V_T/I_2) \ln(NI_1/I_2)$ . With  $I_{S1} = 0.05$  pA,  $N = 10$ ,  $V_T = 25$  mV,  $I_1 = 2$  mA,  $I_2 = 10$  mA, we find  $R = 1.73 \Omega$ .

[2]

c) With  $V_{OUT} = 5$  V and a  $50 \Omega$  load, Q2 has an emitter current of  $I_{E2} = 100$  mA. The base-emitter voltage of Q2 under these conditions is  $V_{BE2} = V_T \ln(\alpha I_{E2}/I_{S2}) = 650$  mV. The emitter current of Q1 is  $I_{E1} = I_1 - I_{E2}/(1 + \beta) = 2 - 100/101 = 1.01$  mA, and its base-emitter voltage is  $V_{BE1} = V_T \ln(\alpha I_{E1}/I_{S1}) = 593$  mV. The input voltage is  $V_{in} = V_{out} + I_{E2} R + V_{BE2} - V_{BE1}$ , which gives  $V_{in} = 5.23$  V. The voltage gain is therefore  $V_{out}/V_{in} = 0.956$ .

[7]

d) With  $V_{OUT} = 10$  V, the emitter currents of Q2 and Q1 are  $I_{E2} = 200$  mA and  $I_{E1} = 0.02$  mA respectively (almost at limit of output range). Repeating the above calculations in this case gives  $V_{BE2} = 668$  mV,  $V_{BE1} = 495$  mV,  $V_{in} = 10.52$  V, and  $V_{out}/V_{in} = 0.951$ .

The amplifier appears to be linear to within  $\approx 0.5\%$ , based on the gains at 50% and 100% of full scale output. However, the comparison doesn't tell us anything about the residual cross-over distortion.

[3]