

Paper Number(s): **E2.1**

IMPERIAL COLLEGE OF SCIENCE, TECHNOLOGY AND MEDICINE
UNIVERSITY OF LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
EXAMINATIONS 2009

EEE/ISE PART II: MEng, BEng and ACGI

DIGITAL ELECTRONICS 2

Thursday, 28 May 2:00 pm

There are FOUR questions on this paper.

Q1 is compulsory.

Answer Q1 and any two of questions 2-4.

Q1 carries 40% of the marks. Questions 2 to 4 carry equal marks (30% each).

Time allowed: 2:00 hours

Examiners responsible:

First Marker(s): D.M. Brookes D.M. Brookes

Second Marker(s): T.J.W. Clarke T.J.W. Clarke

Information for Candidates:

Notation: *Unless explicitly indicated otherwise, digital circuits throughout this paper are drawn with their inputs on the left and their outputs on the right. The notation $X2:0$ denotes the three-bit number $X2$, $X1$ and $X0$. The least significant bit of a binary number is always designated bit 0. Signed binary numbers use 2's complement notation.*

1. (a) *Figure 1.1* shows the state diagram for a state machine which has a single input, A, a single output, X, and a state that is represented by the value of the unsigned 2-bit number S1:0. State transitions occur on the rising edges of CLOCK which, for convenience, have been shown as numbered dashed lines in the timing diagram of *Figure 1.1*.

(i) Draw the state table for the circuit. [3]

(ii) Complete the timing diagram shown in *Figure 1.1* by showing the state of the circuit during each clock cycle as a decimal number and the waveform of X. The state machine is initially in state 0 as shown. [5]

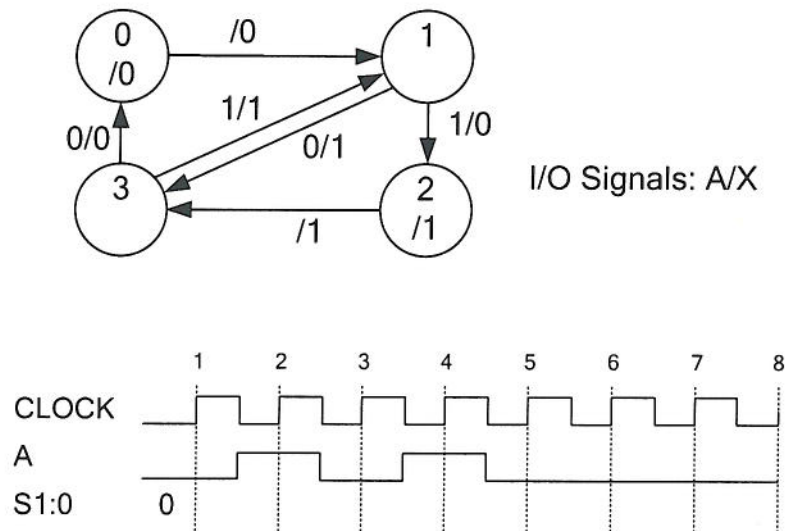


Figure 1.1

- (b) In the circuit of *Figure 1.2* the propagation delays of the leftmost flipflop and the logic block are t_p and t_d respectively. The rightmost flipflop has setup and hold times of t_s and t_h . The clock signal C is symmetrical with period T .

(i) Write the setup and hold inequalities that apply to the rightmost flip-flop. [5]

(ii) Find the maximum clock frequency for the circuit if the timing parameters (in ns) are: $t_p = 6$, $t_s = 5$, $t_h = 2$ and $15 \leq t_d \leq 27$. [3]

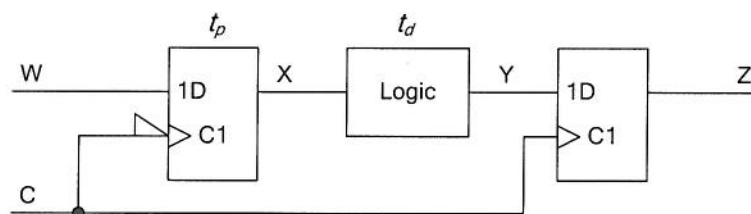


Figure 1.2

- (c) Figure 1.3 shows a successive-approximation analogue-to-digital converter preceded by a sample/hold circuit formed from an op-amp, an electronic switch and a capacitor. The converter has 14 bits precision and a full scale input range of $\pm 5\text{ V}$.

If the A/D input current lies in the range $\pm 20\text{ nA}$, calculate the minimum value of C to ensure that V_C does not vary by more than $\frac{1}{2}\text{ LSB}$ during the $2\mu\text{s}$ conversion time.

[8]

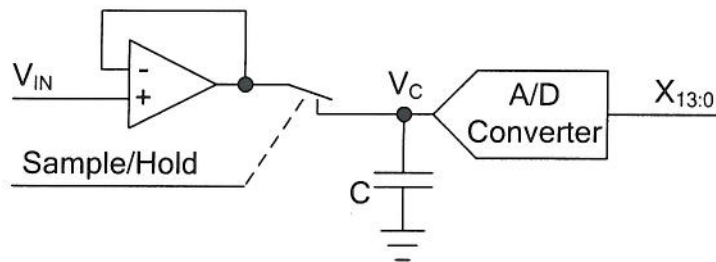


Figure 1.3

- (d) Figure 1.4 shows a circuit containing a 4-bit full adder. $X_3:0$ and $Y_6:0$ are unsigned binary numbers whose values are x and y respectively.

- Show that $y = 5x$.
- Determine the maximum possible value of y .
- If $X_3:0$ is now a signed two's complement binary number whose value is x , give the maximum and minimum values of $y = 5x$.
- Show how the circuit must be modified to calculate $y = 5x$ correctly when $X_3:0$ is a signed number as in part (iii).

[2]

[2]

[2]

[2]

 


Figure 1.4

- (e) X7:0 is an 8-bit signed number in the range -128 to +127. Determine the decimal number range or ranges of values of X7:0 for which the following expressions are true:

(i) $\overline{X7} \cdot \overline{X6} \cdot X5 \cdot X4$

[4]

(ii) $(\overline{X7} \oplus X6) \cdot (\overline{X7} \oplus X5)$

[4]

3. The circuit of *Figure 3.1* forms part of a bit-serial data transmission system. The input D is synchronized to the CLOCK and represents the sequence of bits to be transmitted. The outputs POS and NEG cause positive and negative pulses to be transmitted respectively. The 2-bit counter labelled CTR2 increments on each rising edge of CLOCK unless D is high in which case it resets to zero. The counter outputs and register outputs are all initially zero as shown in the timing diagram.
- Explain why the counter does not increment to 1 until cycle 4 of the diagram and show its value in the remaining clock cycles. [6]
 - Explain the circumstances under which L changes state and complete its waveform for the remaining clock cycles. [7]
 - Draw the waveform of G and hence draw the waveforms of POS and NEG for all the remaining clock cycles. [12]
 - Explain why there will be at least one pulse on either POS or NEG every four clock cycles. [5]

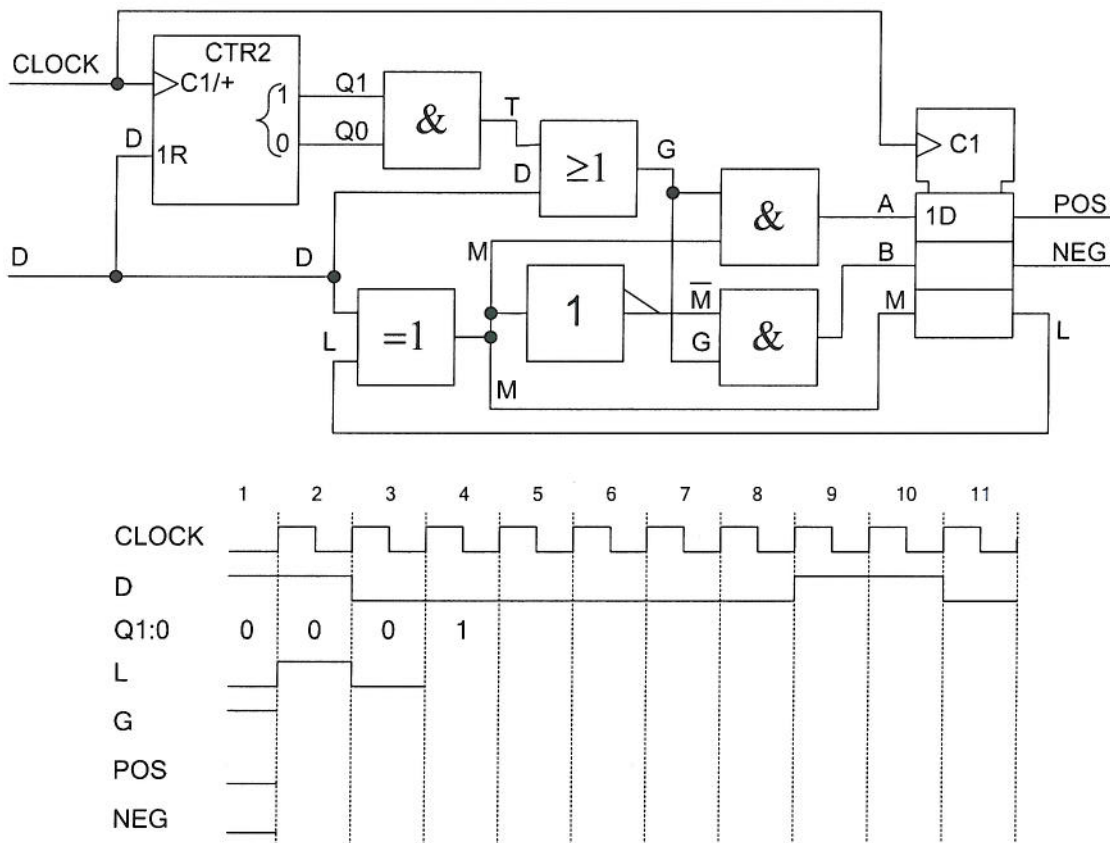


Figure 3.1

4. (a) Show that the two circuits in *Figure 4.1* calculate the same Boolean expression for Y and explain what is meant by saying that the circled pair of signals in the rightmost circuit form an “AND bundle” representation for \overline{X} . [4]
- (b) The circuit of *Figure 4.2* includes a multiplexer whose input and output signals are “AND bundles” as shown. Show that the multiplexer can be implemented using only NAND gates and inverters with propagation delays of 2 gate delays from the SEL input and 1 gate delay from the other inputs. [8]
- (c) *Figure 4.2* shows the circuit of a “carry-skip” adder which includes an n -bit full adder whose propagation delays (in gate delay units) are as follows:


2009 E2.1/ISE2.2 Solutions

Key to letters on mark scheme: B=Bookwork, C=New computed example, A=Analysis of new circuit, D=design of new circuit

1. (a) (i)

Next State/X		A=0	A=1
State	0	1/0	1/0
	1	3/1	2/0
	2	3/1	3/1
	3	0/0	1/1

[3A]

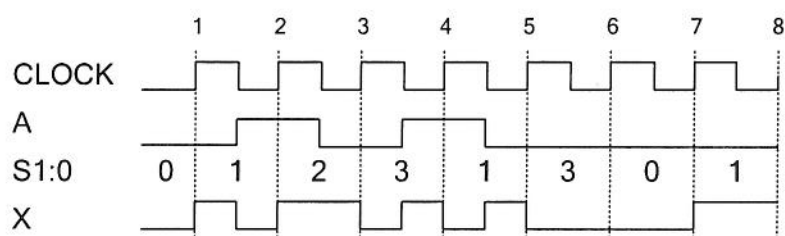

[5A]

(b) Taking a falling edge as the time reference, the setup equation is:

$$t_p + t_d + t_s < \frac{1}{2}T \Rightarrow 6 + 27 + 5 < \frac{1}{2}T \Rightarrow T > 76$$

The hold time equation is:

$$t_h < t_p + t_d + \frac{1}{2}T \Rightarrow 2 - 6 - 15 < \frac{1}{2}T \Rightarrow T > -38$$

[5A]

$$\text{Hence } T > 76 \text{ ns} \Rightarrow f < 13.16 \text{ MHz}$$

[3C]

$$(c) \quad \frac{dV}{dt} = \frac{I}{C} \Rightarrow C = \frac{Idt}{dV} = \frac{20\text{n} \times 2\mu}{10 \times \frac{1}{2} \times 2^{-14}} = \frac{40\text{f}}{305\mu} = 131\text{pF}$$

[8A]

- (d) (i) To multiply by 5, we calculate $x + 4x$ and obtain the multiplication by 4 by shifting left by two bits: [2A]

$$\begin{array}{rcccccc} & X3 & X2 & X1 & X0 & 0 & 0 \\ + & & & & X3 & X2 & X1 & X0 \\ \hline \end{array}$$

The two LSBs of this sum do not require any logic and so we can use a 4-bit adder for the rest of the bits. Because the addition is unsigned, we can use CO as a fifth output bit.

- (ii) The maximum possible value of x is 15, so the maximum value of y is $15 \times 5 = 75$ (1001011 in binary) which requires 7 bits. [2A]
- (iii) The range of x is now -8 to $+7$, so the range of y is -40 to $+35$. [2A]
- (iv) We need to sign-extend the Q input instead of zero-padding it. If P and Q were independent inputs, we would also need to use a full 5-bit adder. However, in this case, P and Q always have the same sign and so the CO gives the correct value for Y6. [No penalty for using a full 5-bit adder]. In fact, Y6 always equals X3 also. [2D]


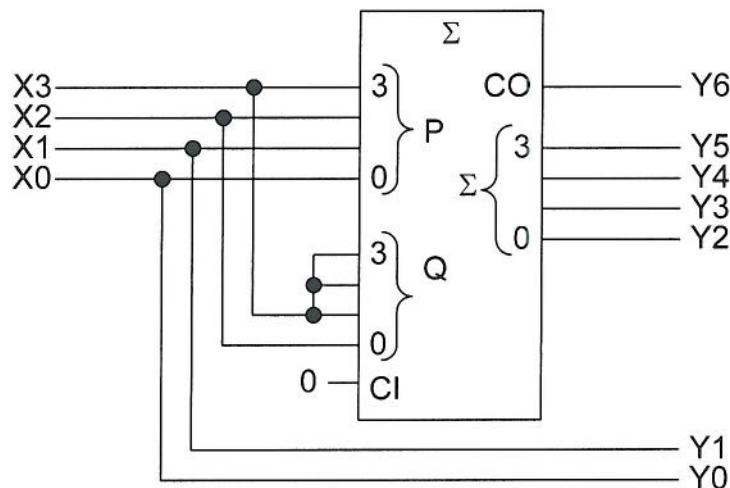



Figure 1.4

- (e) (i) This expression is true for the binary range 00110000 to 00111111 which, in decimal, is 48 to 63. [4C]
- (ii) The first term is true when $X7=X6$ and the second when $X7=X5$. This both terms are true iff $X7=X6=X5$. This is true for the binary number range 11100000 to 00011111 which, in decimal, is -32 to $+31$. [4C]

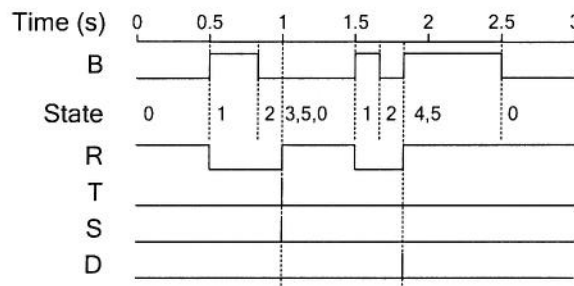
2. (a) When R is high, the counter will remain reset. When R goes low, the counter will start counting and when it reaches 512, Q9 (=T) will go high; this will be 0.512 seconds after R went low. Since T now is high, the count enable input (labelled G2) will be low and the counter will remain at 512 until it is reset on the clock cycle after R goes high. The counter is now held at zero until R goes low when the whole process starts again. [8A]
- (b) After the first pulse the state machine remains in state 2 until T goes high 0.514 s after the start of the pulse. At this point, T goes high and the state machine goes to state 3 and emits an S pulse. In the second sequence, however, B goes high before the 0.513 s has elapsed and so the state machine goes into state 4 and emits a D pulse. [12A]



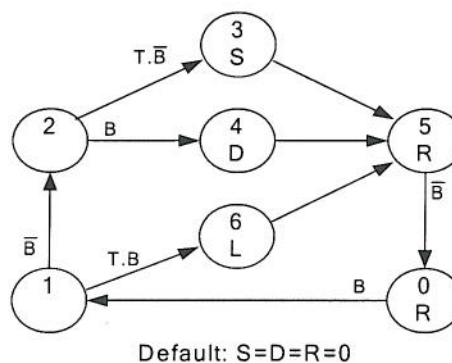- (c) If B goes high on CLOCK rising edge 0 at $t = 0.5$ s, R will go low just after edge 1 and so the counter will count to 1 after edge 2 and to 512 after edge 513. Therefore T will go high just after edge 513. The state machine will therefore enter state 3 at edge 514 causing S to go high. This therefore happens at $t = 1.014$ s. [5A]
- (d) To detect a long press, we introduce an extra state and branch to it if T goes high while we are in state 1. [Other solutions including a Mealy machine are possible]. [5D]



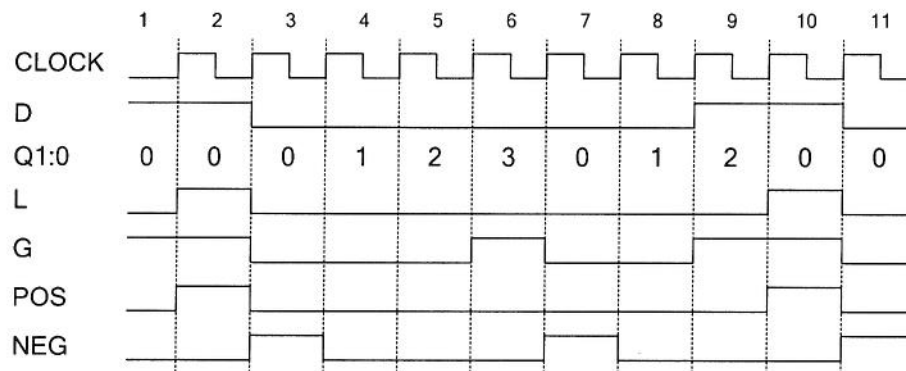
3. (a) The counter is held reset as long as D remains high. D goes low just after the CLOCK rising edge and so the counter cannot increment to 1 until the following rising edge. [6A]
- (b) Since $M = L \oplus D$, L will change state at the end of any clock cycle in which D is high, i.e. at the end of cycles 1, 2, 9 and 10. [7A]
- (c) G is true whenever D is true and also whenever $Q_{1:0}=3$. Whenever G is high, either A or B will also be high depending on whether M is high or low. Therefore there will be a pulse on either POS or NEG during the following cycle. Since M also determines the value of L in the following cycle, L will be high during a POS pulse and low during a NEG pulse. [12A]
- (d) When D is low, the counter runs and G will go high every fourth clock cycle when the counter equals 3. When D is high, then G is also forced high. Thus G can never be low for more than three consecutive clock cycles. Whenever G is high, there is a POS or NEG pulse during the next clock cycle. It follows that there can never be more than 3 consecutive clock cycles without a POS or NEG pulse. [5A]



- 4 (a) The central NAND gate and inverter can be merged to form an AND gate. We then have an AND gate feeding an NAND gate which is equivalent to a single 3-input NAND gate as in the rightmost circuit. Also easily shown using Boolean algebra. [4A]

We know, from the first circuit, that the NAND of the two circled signals is X , and so their AND is \overline{X} . An “AND bundle” is a group of signals whose AND represents a signal in the circuit that is significant but that is never explicitly formed.

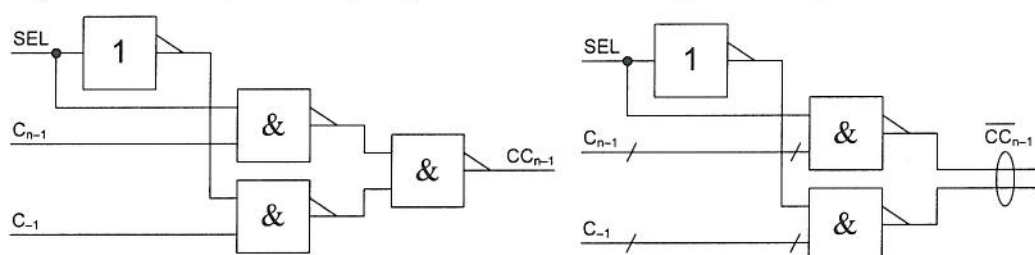- (b) The left circuit shows a conventional multiplexer formed from NAND gates. We can omit the final NAND gate to give an AND bundle output of $\overline{CC_{n-1}}$ and the bundled inputs just increase the number of inputs required for the other NAND gates. The delay is clearly 2 gates from the SEL input and 1 gate from the others. [8D]



- (c) If $SEL=1$, then the multiplexer selects C_{n-1} as its input and so $CC_{n-1} = C_{n-1}$. $SEL=0$ only occurs when each of the XOR terms in the expression for SEL is true, i.e. when each column of the addition is propagating the carry. Under these circumstances, $C_{n-1} = C_{-1}$ and so $CC_{n-1} = C_{n-1}$ is true for this case as well. The delays are now as given below: [10A]

Gate delays		Output	
		$\overline{CC_{n-1}}$	S
Input	C_{-1}	1	$n+3$
	P	$\max(5, n+2)$	$n+3$

The delays to S are unaffected by the addition of the multiplexer. The delay from C_{-1} to $\overline{CC_{n-1}}$ is only 1 gate, while the delay from P now has two paths: one via SEL with a delay of $2+1+2=5$ and one via C_{n-1} which now has an additional 1-gate delay introduced by the multiplexer.

- (d) We can calculate the delays to the S outputs by adding appropriate values from the table calculated in part (c). [3C]
- (i) From the table given in the question: delay is $64+3=67$. [5C]
- (ii) Worst case is $P0 \rightarrow C7 \rightarrow C15 \rightarrow \dots \rightarrow C55 \rightarrow S63 = 10 + 6 \times 1 + 11 = 27$