

MSc and EEE PART IV: MEng and ACGI

Time allowed: 3:00 hours

Answer ALL questions.

All questions carry equal marks

Examiners responsible First Marker(s) : C. Papavassiliou
Second Marker(s) : P. Georgiou

The Questions

1. (a) Explain briefly the role of the oscillator in a superheterodyne receiver. [3]
- (b) Define the noise factor for an electronic system and give an equation for it. [2]
- (c) The input referred noise of an electronic system integrated within a 1KHz band is $100\mu\text{V}^2$. This system is connected to a source which has a total input noise of $2\mu\text{V}^2$ within a 100Hz band. Assuming that all the noise sources are white, what is the noise factor of the system? [3]
- (d) A double superheterodyne receiver is designed using two local oscillators, one of them providing a single tone harmonic at 1MHz, and the second one providing a single tone harmonic at 100KHz. However, in the fabricated circuit the measured first oscillator frequency is 990KHz and the measured second oscillator frequency is 90KHz.
- i) Calculate the value of the first and second IF frequencies (i.e. the IF frequencies after mixing with the first and second oscillators) for an RF signal of 500KHz.
- ii) How does the value of the second IF frequency differ from the originally intended one?
- iii) Based on your answer, mention one advantage double superheterodyne receivers have over single superheterodyne receivers. [6]
- (e) A single superheterodyne receiver is designed to receive RF signals centered at 4MHz with a 500KHz bandwidth. The frequency of the local oscillator is 12MHz. A first order low pass filter is used to attenuate the image signal before mixing with the local oscillator. The cutoff frequency of the filter is 10MHz and its passband gain 0dB.
- i) Where in the frequency spectrum is the image signal?
- ii) What is the attenuation of the image signal in the middle of its frequency range?
- iii) What would you modify in the filter to improve image rejection? [6]

2. For the circuit in Figure 2.1, where all the transistors are equally sized and operating in the strong inversion saturation region:

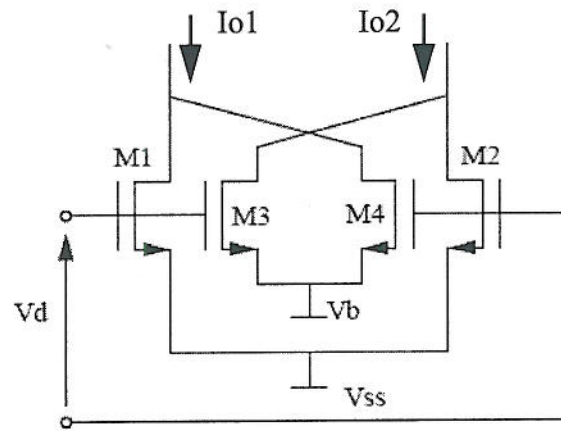


Figure 2.1

(a) Find an expression for the output current $I_{out} = (I_{o1} - I_{o2})$ as a function of transistor voltages V_b , V_{ss} and V_d .

[4]

(b) Draw a schematic to indicate how this circuit could be used as a mixer with differential inputs V_{in1} and V_{in2} . Assume that there are no special requirements on the input impedances for both inputs.

[3]

(c) If V_b is set to 0.5V and V_{ss} to 0V, find the β (transconductance parameter) value of the transistors necessary to implement a transconductor with a transconductance of 100mS.

[4]

(d) Assuming that the value of β calculated in (c) is fixed, calculate the voltage that needs to be applied to V_{ss} in order to reduce the transconductance by a factor of 2.

[3]

(e) Explain how you would build an integrator using a fully differential transconductor and two identical capacitors in order to minimize the effects caused by parasitic capacitances. Draw a schematic of such an integrator.

[3]

(f) Explain briefly how transconductors and capacitors can be used to design LC ladder filters.

[3]

This page is intentionally left blank.

3.

(a) Draw the schematic diagram of a fully linearised differential transconductor using four MOS transistors operating in the strong inversion triode region. Derive an expression for the transconductance of this circuit.

[4]

(b) Is the transconductor in Fig. 3.1 a fully linear transconductor? (Hint: M1 and M2 are operating in the strong inversion saturation region and M3 in the strong inversion ohmic region. $V_{in} = (V_{in1} - V_{in2})$ and $I_{out} = (I_{o1} - I_{o2})$).

Justify your answer. If your answer is "YES" give an expression for the transconductance. If your answer is "NO" explain which circuit technique you would use to linearise it.

[4]

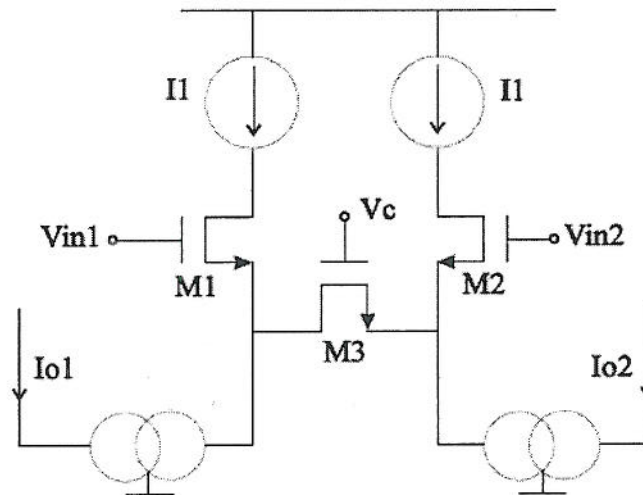


Figure 3.1

Figure 3.2 shows the schematic of a fully differential transconductor where: M1 is operating in the strong inversion ohmic region; M2 and M3 are both equally sized and operate in the strong inversion saturation region; M4, Ma1 and Ma3 operate in the strong inversion saturation region; M3 and Ma3 are equally sized; M4 and Ma1r are equally sized; and N2 is an ideal voltage amplifier. Based on this:

(c) Give an expression for the current flowing through M1, as a function of the transistor's parameters, V_{1p} and V_b .

[3]

4. For the circuit in Figure 4.1:

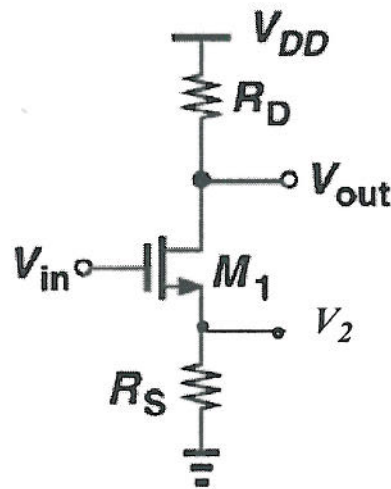


Figure 4.1

(a) Draw the small signal equivalent circuit. You can assume that the output resistance of the transistor is much larger than any other resistance in the circuit.

[3]

(b) Analyse the equivalent circuit from (a) and find an expression for the gain V_{out}/V_{in} .

[4]

(c) Draw the small signal equivalent circuit including all possible noise sources, and give expressions for them.

[4]

(d) Find the equivalent noise power spectral density at the input of the circuit. Assume that the circuit operates in a frequency range where for the transistor flicker noise dominates. Assume also that the noise contribution due to the passive resistors is at least the same order of magnitude as the flicker noise of the transistor.

[3]

(e) Find the equivalent noise power spectral density in node V_2 .

[3]

(f) A low pass filter is connected at the output (V_{out}) of the circuit with transfer function

$$H(s) = \frac{1}{1 + \left(\frac{s}{10^6}\right)}$$

Give an expression for the total noise power at the input of the filter in a 5Hz to 6GHz bandwidth.

[3]

Department of Electrical and Electronic Engineering Examinations 2011 Confidential			
Model Answers and Mark Schemes		First Examiner:	Esther Rodriguez-Villegas
Paper Code:	E4.17	Second Examiner:	Christos Pappavassiliou

1.

(a) (Theory)

If we are trying to select one particular frequency channel from the complete RF spectrum, then we need a bandpass filter to reject any unwanted frequencies. Generally this filter has to be narrowband, and high Q filters are difficult to design at high frequencies. This problem is compounded if the input signal frequency is variable (i.e. the signal is transmitted in one of a number of possible channels, each with the same bandwidth). A tuneable, high Q bandpass filter with constant bandwidth is now required.

The solution is to use a superhet receiver (supersonic heterodyne). This system downconverts the input signal to an intermediate frequency (IF), and a bandpass IF filter is then used to select the wanted signal. The design of the bandpass IF filter is eased since it doesn't have to be tuneable, and the IF centre frequency is much lower than the input RF signal.

The downconversion is performed by 'mixing' (multiplying) the RF input signal (f_{RF}) with a local oscillator signal (f_{LO}), such that the resulting output is at the required IF frequency (f_{IF}).

The oscillator frequency f_{LO} is often tuneable to ensure that a range of input RF frequencies can be selected.

(b) (Theory)

Noise factor is defined as the total output (or input) noise power of the system divided by the output (or input) noise power due to the source alone (P_{ni}).

$$\text{Noise factor } F = (P_{sys} + P_{ni})/P_{ni}$$

(c) (Application of theory)

The noise factor must be calculated using the same bandwidth for the system and the source. If all the sources are white, it means that the power spectral densities are, $100\text{nV}^2/\text{Hz}$ and $20\text{nV}^2/\text{Hz}$. Therefore, using the formula in (b) the noise factor is 6.

Department of Electrical and Electronic Engineering Examinations 2011 Confidential

Model Answers and Mark Schemes

First Examiner:

Esther Rodriguez-Villegas

Paper Code: E4.17

Second Examiner:

Christos Pappavassiliou

(d) (Application of theory)

First IF is at $(990\text{kHz} - 500\text{kHz}) = 490\text{kHz}$

Second IF is at $(490\text{kHz} - 90\text{kHz}) = 400\text{kHz}$

There is no difference with the originally intended one. One of the advantages of double superheterodyne receivers is that if the second local oscillator can be designed such that it tracks any frequency offsets or drift of the first LO, then the effects of these frequency offsets can be minimised.

(e) (Application of theory)

The image signal would be centered at 20MHz, with a frequency range from 19.75MHz to 20.25MHz. The attenuation would be 23dB. To improve the attenuation of the image the filter could be designed with a lower cut-off frequency.

Department of Electrical and Electronic Engineering Examinations 2011 Confidential

Model Answers and Mark Schemes

First Examiner:

Esther Rodriguez-Villegas

Paper Code: E4.17

Second Examiner:

Christos Pappavassiliou

2.

(a) (Theory)

$$I_{d1} - I_{d2} = \beta V_d (V_{c1} - V_{th}) \quad I_{d3} - I_{d4} = \beta V_d (V_{c2} - V_{th})$$

$$\text{where } V_{c1} = \frac{V_{gs1} + V_{gs2}}{2} \text{ and } V_{c2} = \frac{V_{gs3} + V_{gs4}}{2}$$

$$\begin{aligned} \text{Thus } I_{out} &= (I_{d1} - I_{d2}) - (I_{d3} - I_{d4}) \\ &= \beta V_d (V_{c1} - V_{c2}) = \beta V_d (V_b - V_{ss}) \end{aligned}$$

(b) (Application of theory)

V_{in1} can be connected as V_d and V_{in2} between V_d and V_{ss} , or viceversa.

(c) (Computed example)

The transconductance is given by:

$$G_m = \beta (V_b - V_{ss}). \text{ From there, } \beta \text{ should be } 200 \text{ mA/V.}$$

(d) (Computed example)

Once β is fixed, in order to reduce the transconductance, the difference between V_b and V_{ss} has to be also reduced. In this case $V_{ss}=0.25\text{V}$.

Department of Electrical and Electronic Engineering Examinations 2011 Confidential

Model Answers and Mark Schemes

First Examiner:


Esther Rodriguez-Villegas

Paper Code: E4.17

Second Examiner:

Christos Pappavassiliou


(e) (Theory)

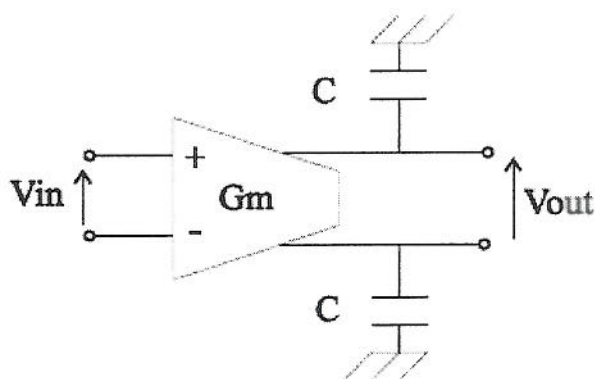

Alternatively the two capacitors could be connected in parallel across V_{out} , but with their top and bottom plates inverted.

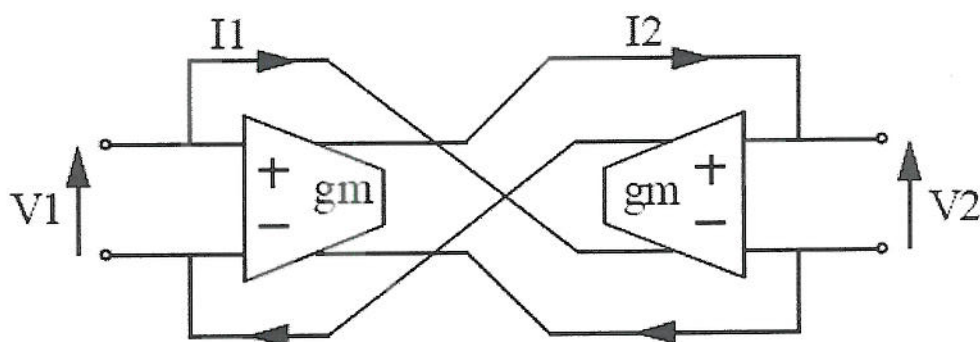(f) (Theory)

Substituting the inductors in the ladder by gyrators:



Department of Electrical and Electronic Engineering Examinations 2011 Confidential

Model Answers and Mark Schemes

First Examiner:

Esther Rodriguez-Villegas


Paper Code: E4.17

Second Examiner:

Christos Pappavassiliou

3.

(a) (Theory)

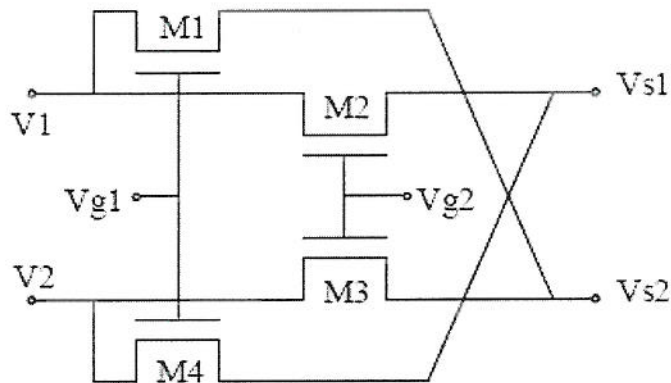

If $V_{s1}=V_{s2}=V_s$

$$I_{d1} = G_1(V_1 - V_s) - \beta (V_1 - V_s)^2$$

$$I_{d2} = G_2(V_1 - V_s) - \beta (V_1 - V_s)^2$$

$$I_{d3} = G_2(V_2 - V_s) - \beta (V_2 - V_s)^2$$

$$I_{d4} = G_1(V_2 - V_s) - \beta (V_2 - V_s)^2$$

$$\text{where } G_1 = 2\beta(V_{g1} - V_{th}) \quad G_2 = 2\beta(V_{g2} - V_{th})$$

$$I_1 - I_2 = (I_{d1} + I_{d3}) - (I_{d2} + I_{d4})$$

$$= (G_1 - G_2)(V_1 - V_2)$$

And the transconductance is:

$$G_m = 2\beta(V_{g1} - V_{g2})$$

(b) (Application of theory)

No,

$$I_{out} = 2 I_{d3} = 4\beta(V_{gs3} - V_{th})V_{in} - 2\beta V_{in}^2$$

It can be linearised using a cross-couple configuration instead.

Department of Electrical and Electronic Engineering Examinations 2011 Confidential		
Model Answers and Mark Schemes	First Examiner:	Esther Rodriguez-Villegas
Paper Code: E4.17	Second Examiner:	Christos Pappavassiliou

(c) (New theory)

$$I_1 = \beta_1(V_{1p} - V_T)V_b$$

(d) (New theory)

The same as in (c) for all of them.

(e) (New theory)

$$I_{out} = (I_{a3} - I_{a1})$$

Since it is a fully differential configuration, the current in Ma1r is the same as in Ma1, but with V_{1n} in the expression instead. Hence:

$$I_{out} = \beta_1(V_{1p} - V_{1n})V_b$$

(f) $G_m = \beta_1 V_b$

Department of Electrical and Electronic Engineering Examinations 2011 Confidential

Model Answers and Mark Schemes

First Examiner:

Esther Rodriguez-Villegas


Paper Code: E4.17

Second Examiner:

Christos Pappavassiliou

4.

(a) (New theory)

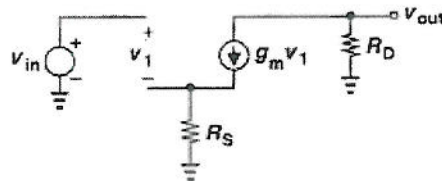

(b) (New theory)

$$A_v = \frac{v_{out}}{v_{in}} = -\frac{g_m R_D}{1 + g_m R_S}$$

(c) (New theory)

The new schematic would be as in (a) but with a current (or voltage) noise source from v_{out} to v_2 that accounts for the thermal noise in the channel plus a voltage noise source at the input that accounts for the flicker noise of the transistor. Another voltage noise source in v_2 (or negative terminal of v_1) that represents the thermal noise of R_S , and another voltage noise source in v_{out} which represents the thermal noise of R_D .

The expressions are;

Thermal between drain and source, i.e. between v_{out} and v_2 : $ind^2 = \frac{8kTgm}{3} \left(\frac{A^2}{Hz} \right)$

Flicker in series with the gate: $vng^2 = \frac{k_f}{C_{ox}WLf} \left(\frac{V^2}{Hz} \right)$

Thermal due to R_D : $v_{RD}^2 = 4kTR_D \left(\frac{V^2}{Hz} \right)$

Thermal due to R_S : $i_{Rs}^2 = 4kTR_s \left(\frac{V^2}{Hz} \right)$

Department of Electrical and Electronic Engineering Examinations 2011 Confidential

Model Answers and Mark Schemes

First Examiner:

Esther Rodriguez-Villegas

Paper Code: E4.17

Second Examiner:

Christos Pappavassiliou

(d) (New theory)

Since the Flicker noise dominates in the transistor, thermal noise does not need to be considered. The noise contribution of the Flicker noise, is already at the input of the circuit, so it is just a matter of transferring the other two sources of noise (i.e. the ones generated by R_D and R_s) back to the input. The noise generated by R_D is already at the output so, the equivalent at the input can be found dividing by the power gain between input and output, i.e. the square value of the expression calculated in (b):

$$v_{RD(input)}^2 = \frac{4kTR_D}{A_v^2} \left(\frac{V^2}{Hz} \right)$$

And for R_s , first the power gain from V_2 to V_{in} has to be found from the circuit in (a):

$$g_m(v_{in} - v_2) = \frac{v_2}{R_s}, \text{ and from here:}$$

$$v_{Rs(input)}^2 = \frac{4kTR_s \left(g_m + \frac{1}{R_s} \right)^2}{g_m^2} \left(\frac{V^2}{Hz} \right)$$

The total power spectral density of noise at the input is:

$$P_{input} = \left[\frac{k_f}{C_{ox}WLf} + \frac{4kTR_D}{A_v^2} + \frac{4kTR_s \left(g_m + \frac{1}{R_s} \right)^2}{g_m^2} \right] \left(\frac{V^2}{Hz} \right)$$

(e) (New theory)

Using the result in (d), and the power gain from V_{in} to V_2 :

$$P_{V_2} = \left[\frac{k_f}{C_{ox}WLf} + \frac{4kTR_D}{A_v^2} + \frac{4kTR_s \left(g_m + \frac{1}{R_s} \right)^2}{g_m^2} \right] \left(\frac{g_m}{g_m + \frac{1}{R_s}} \right)^2 \left(\frac{V^2}{Hz} \right)$$

Department of Electrical and Electronic Engineering Examinations 2011 Confidential

Model Answers and Mark Schemes

First Examiner:

Esther Rodriguez-Villegas

Paper Code: E4.17

Second Examiner:

Christos Pappavassiliou

(f) (New theory and computed example)

The filter has no influence in the power spectral density within that band, since the cutoff frequency is at a much larger frequency. Based on that it is a matter of integrating the expression in (d) using as integration limits 6Hz and 5Hz:

$$\text{Noise}_{\text{input}} = \left[\frac{k_f}{C_{\text{ox}} W L f} \ln\left(\frac{6}{5}\right) + \frac{4kTR_D}{A_v^2} + \frac{4kTR_s \left(g_m + \frac{1}{R_s}\right)^2}{g_m^2} \right] (V^2)$$