

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATIONS 2012

MSc and EEE PART III/IV: MEng, BEng and ACGI

Corrected Copy



**ANALOGUE INTEGRATED CIRCUITS AND SYSTEMS**

Monday, 30 April 2:30 pm

Time allowed: 3:00 hours

Correction

Q5b 2.45pm

**There are SIX questions on this paper.**

**Answer FOUR questions.**

Q4 c(iv) 4.25pm

*All questions carry equal marks*

**Any special instructions for invigilators and information for candidates are on page 1.**

Examiners responsible      First Marker(s) :      C. Toumazou  
Second Marker(s) :      P. Georgiou

1. Figure 1 below shows a single stage of a differential amplifier.

(a)

(i) Draw a circuit schematic for the current source  $I_0$  that ensures the differential gain is independent of temperature and power supply variation. Include any start up circuits that may be required.

[9]

(ii) For your design, show that the gain bandwidth product is independent of temperature.

[6]

(b) Draw a circuit schematic of a stable voltage reference that could provide the bias voltage  $V_s$  and is independent of temperature variation.

[5]

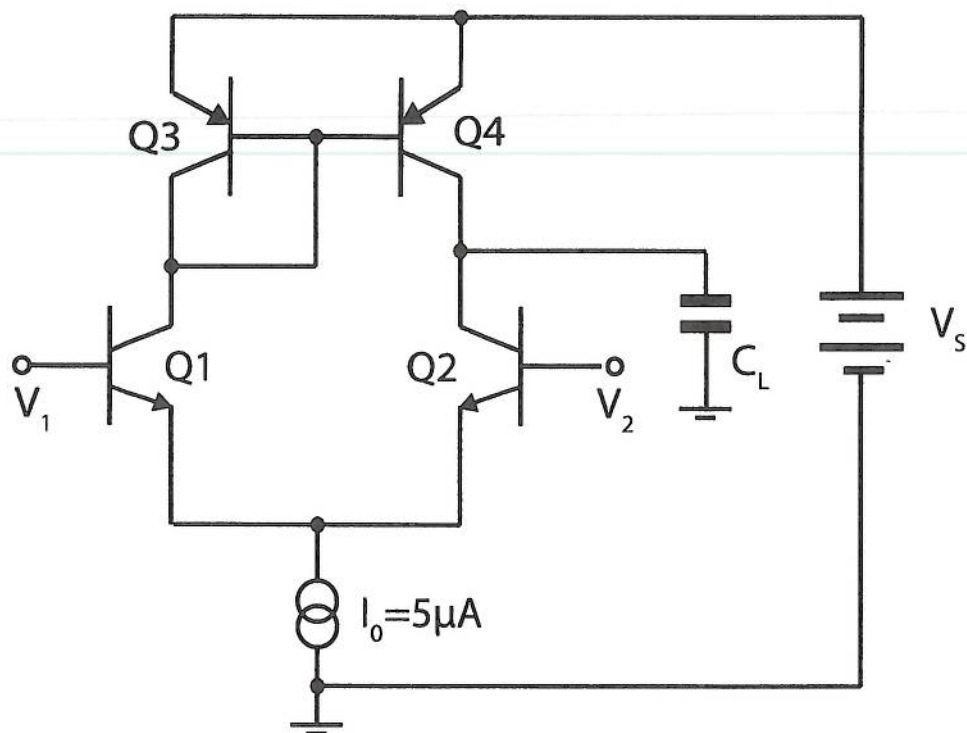


Figure 1.

2. (a). (i) Draw a circuit schematic for a 2-stage voltage mode operational amplifier. [5]  
 (ii) Draw a circuit schematic for a single stage current feedback op-amp. [5]
- (b). Figure 2 below shows a 2-stage non-inverting amplifier, whereby  $R_f$  and  $R_1$  are the gain resistors and  $C_c$  is the compensation capacitor used internally for frequency compensation, which is connected from the output of the first stage to the output of the op-amp.
- (i). The op-amp has a Gain Bandwidth Product of 1MHz and an input trans-conductance  $g_m=50.2\text{mS}$ . Calculate the value of the compensation capacitor  $C_c$ , assuming the Gain Bandwidth is determined by the first pole frequency. [2]
- (ii). Assuming now that the circuit in Figure 2 is a current feedback op-amp with a pole,  $f_{CL}$ , at 10 KHz is given as:
- $$f_{CL} = \frac{1}{2\pi R_f C_c}$$
- Calculate the value of  $R_1$  for the closed loop gain  $A_{CL}=100$  at this frequency. [4]
- (c). Explain why the slew-rate constraints of a current-feedback op-amp are significantly higher than a voltage mode op-amp. [4]

 


Figure 2.

3. (a). Figure 3 shows a two-stage CMOS op-amp.

(i) Estimate the low-frequency differential voltage gain and gain-bandwidth product of the amplifier. Aspect ratios of all devices are shown on the circuit. Assume all bulk effects are negligible. Device model parameters are given below.

[8]

(ii) What is the main advantage and disadvantage of using a single-stage op-amp instead of a two-stage op-amp?

[2]

(b).

(i) Show how the output transistors can be cascoded to increase the voltage gain.

[6]

(ii) State two advantages and two disadvantages of using a cascoded output stage.

[4]

### CMOS TRANSISTOR PARAMETERS

MODEL PARAMETERS	$K_p (\mu A/V^2)$	$\lambda (V^{-1})$	$V_{TO} (V)$
PMOS	20	0.03	-0.8
NMOS	30	0.02	1.0

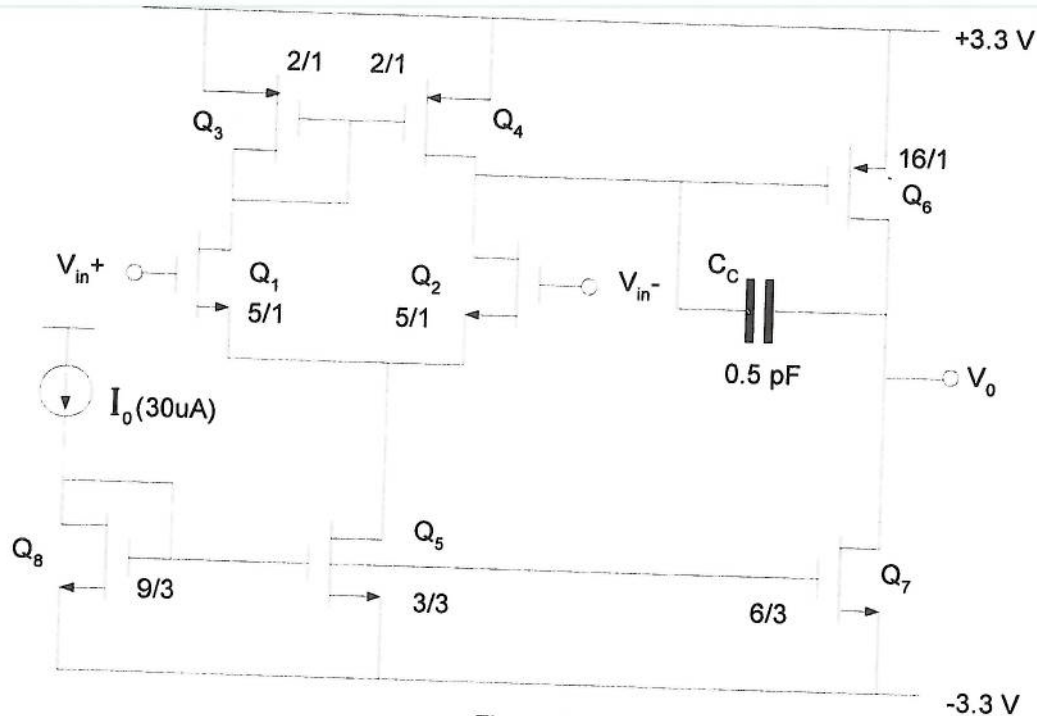


Figure 3

4. Figure 4 shows a differential opamp which is based upon a folded cascode design

(a). Explain what is meant by folded cascode.

[4]

(b). Sketch a circuit diagram of the folded cascode opamp including a circuit which ensures the common mode voltage is maintained at the output.

[6]

(c). (i) Derive the equation for the linear differential resistor of the circuit shown in Figure 4.

[5]

(ii) Assuming the time constant of the circuit is  $\tau=10\text{ms}$ , calculate the value of feedback capacitor,  $C$ , assuming input transistors  $Q_1$  and  $Q_2$  are operating in the triode region and have  $W/L=5$ ,  $K=20\mu\text{A/V}^2$ ,  $V_g=1\text{V}$ ,  $V_t=0.5\text{V}$  and node  $x$  is at a common mode of  $0\text{V}$ . You may neglect any body effects.

[5]

Corrected  
4.25pF

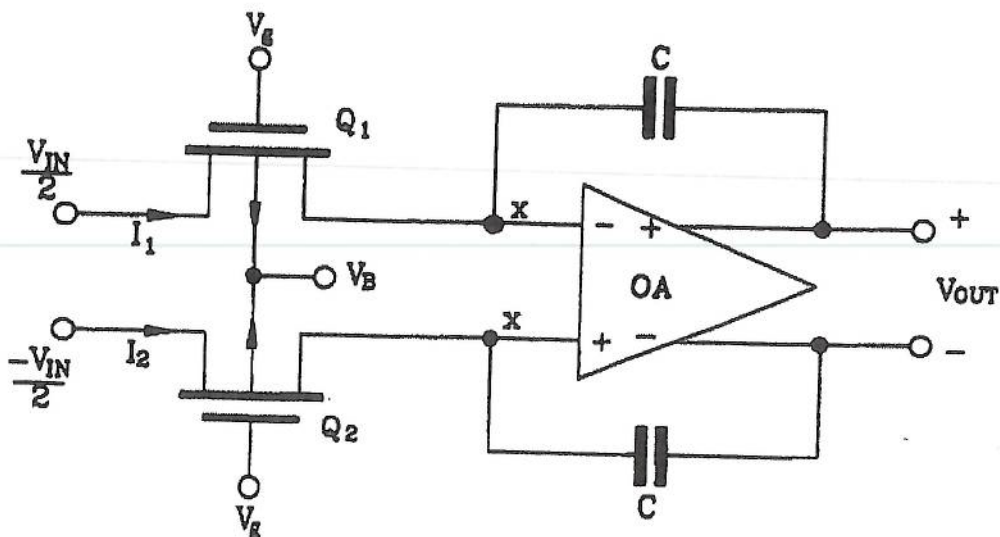


Figure 4.

5. (a) (i) Explain the principles of sigma delta modulation. [5]  
 (ii) Sketch a typical circuit architecture of a sigma delta modulator. [5]
- (b) Figure 5 shows one bit of an algorithmic data converter. *corrected 2.45u*  
 (i) Explain how the data conversion works. [3]  
 (ii) Show how this can be cascaded to perform an 8-bit data conversion. [3]
- (c) What noise limits the resolution of a sampled-data converters? [4]

 


Figure 5.



6. (a) Sketch the basic design of a 3rd-order Chebyshev low pass switched-capacitor ladder filter using op-amps, capacitors and switches.

[5]

- (b) For the circuit in part a. state the equations of the normalised passive component values and draw the equivalent RLC prototype.

[5]


- (c) From the circuit, calculate normalised passive component values for the original double terminated LC prototype of the filter. The filter is to have a cut-off frequency of 5kHz and assume a clocking frequency of 100 kHz. The values of the integration capacitor for the capacitor-based sections are 5.06pF, and for the inductive based sections is 3.49pF. All other switched capacitors are 1pF. All values should be normalised to 1rad/s. You may assume that the clocking frequency is so high that the integrators can be assumed lossless.

[10]

Answers to question 1:

1.a i) Self biased PTAT current source with start up circuit.

1/8

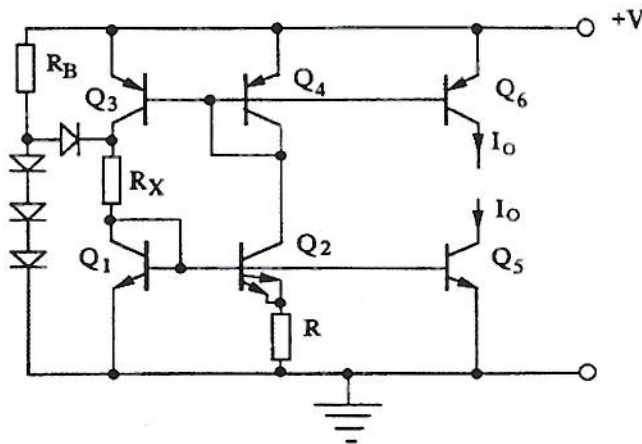

Drawing of PTAT [5]

Drawing of Startup Circuit [4]

ii) Prove that  $g_m$  is independent of temperature and therefore gain bandwidth.

$$GBW = \frac{g_{m2}}{2\pi C_c}$$

$$g_m = \frac{I_0}{V_t}$$

$$I_0 = (V_{be1} - V_{be2}) / R = V_T \ln[I_m / I_0] / R$$


$$I_m / I_0 = 2$$

$$g_m = \frac{V_T \ln[2] / R}{2\pi V_t} = \frac{\ln[2]}{2\pi R}$$

$$GBW = \frac{\ln[2]}{2\pi RC_c}$$

[6]

b. Bandgap voltage reference circuit.

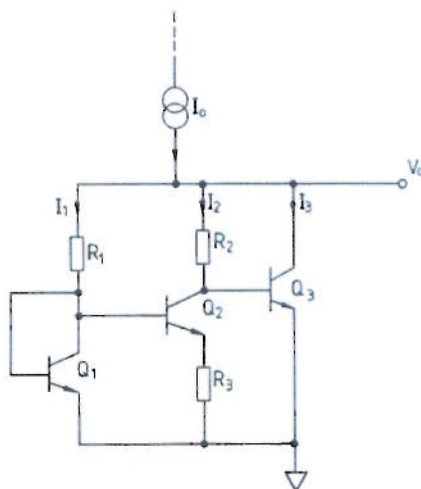


[5]




## Answers to question 2:

### 2. a. 2 stage voltage mode op amp

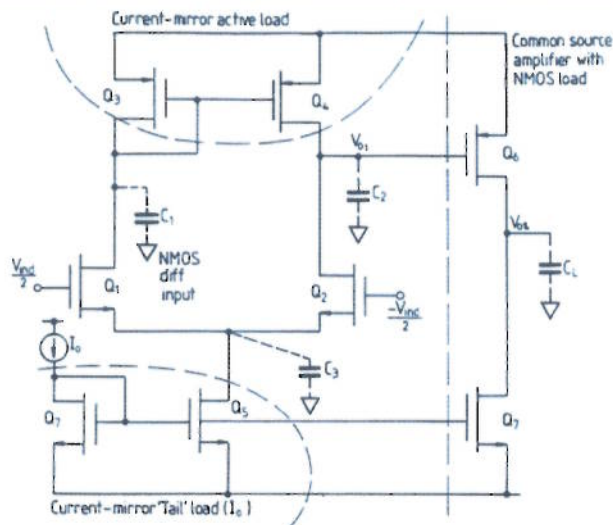

[5]

### Current feedback op amp

 

[5]

$$\text{b. I. } GBW = \frac{g_m}{2\pi C_c} \Rightarrow C_c = \frac{g_m}{2\pi \cdot GBW} = \frac{8 \cdot 10^{-3}}{10^5} = 8 \text{ pf}$$

[2]

II. Student needs to identify that for current feedback op-amps the gain is independent of bandwidth. Therefore:

$$f_{CL} = \frac{1}{2\pi R_f C_c} \Rightarrow R_f = \frac{1}{2\pi f_{CL} C_c} = \frac{1}{2\pi \cdot 10^3 \cdot 8 \cdot 10^{-9}} = 1.99 \text{ K}\Omega$$

$$A_{CL} = (1 + R_f/R_1) \text{ therefore } R_1 = 1990 / 100 - 1 = 20.1 \Omega$$

[4]

c. The two inputs of the CFOA have very different impedance levels compared with the VOA.

$SR = Z_t [\Delta I_{in} / \Delta t]$  where  $I_{in}$  is the current into the low impedance (-ve) input.

Since there is no upper limit on  $\Delta I_{in}/\Delta t$ , the slew rate does not have a maximum value as in the case of a VOA. The large signal bandwidth is thus essentially the same as the small signal bandwidth.

[4]

### Answers to question 3:

3. a.

$$A_{v1} = -gm2 / (go2 + go4)$$

$$(go2 + go4) = I_{D2}(\lambda_N + \lambda_P) = 5 \times 10^{-6} \times 0.05 = 2.5 \times 10^{-7} \Omega^{-1}$$

$$gm2 = 2\sqrt{\beta_2 I_{D2}}$$

$$\beta_2 = \frac{K_N}{2} \left( \frac{W}{L} \right)_2 = 7.5 \times 10^{-5} A/V$$

$$gm2 = 3.87 \times 10^{-5} S$$

$$A_{v1} = -154.9$$

$$A_{v2} = -gm6 / (go7 + go6)$$

$$(go7 + go6) = I_{D6}(\lambda_N + \lambda_P) = 20 \times 10^{-6} \times 0.05 = 10 \times 10^{-7} \Omega^{-1}$$

$$gm6 = 2\sqrt{\beta_6 I_{D6}}$$

$$\beta_6 = \frac{K_N}{2} \left( \frac{W}{L} \right)_6 = 1.6 \times 10^{-4} A/V$$

$$gm6 = 1.13 \times 10^{-4} S$$

$$A_{v2} = -113$$

$$A_{total} = A_{v1} \times A_{v2} = 17503$$

$$G.Bp = gm2 / 2\pi C_c = 12.32 MHz$$

[8]


In a 2-stage opamp the load contributes to the 2<sup>nd</sup> pole hence reducing load increases stability.

With a single-stage, the load forms the dominant pole hence reducing the load increases bandwidth.

[2]

c.

### 2. CASCODED OUTPUT

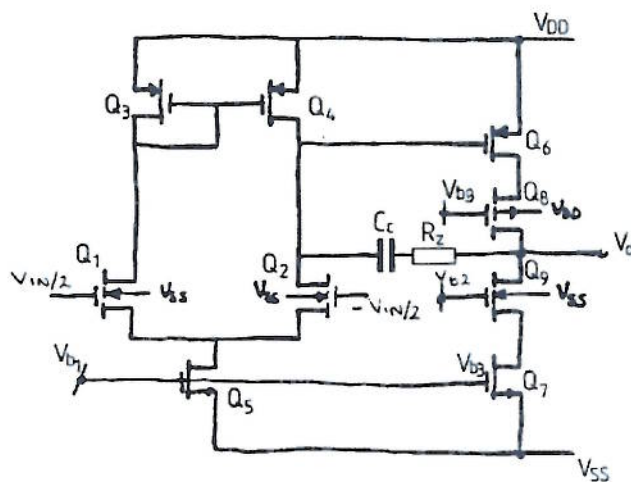

[6]

Cascode output stage increases the output impedance by:

$$G_o = [go6(go8/gm8) + go7(go9/gm9)]$$

$$\text{Since Gain of output stage} = gm6 / [G_o] = A_{v2}$$


The overall gain therefore increases.

[4]

### Answers to question 4:

4.a

#### Concept

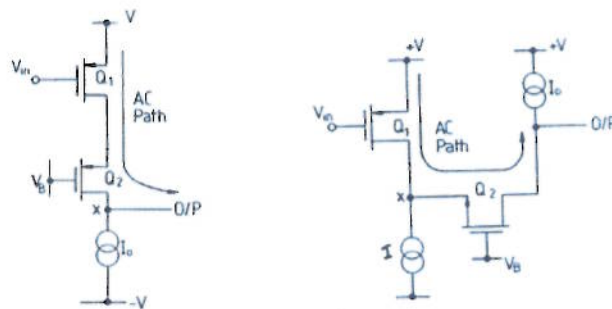

Conventional  
'stacking' cascode


Folded cascode

In the folded cascode we are unstacking the conventional cascode and spreading it out. The AC current path is folded and this allows a reduction in power supply. The conventional cascode requires a 2-stage architecture and since the impedance at (x) is high requires internal compensation. The folded cascode can be used as a single stage architecture, node x is low impedance so the only high impedance node will be at the output.

Gain of the folded cascode  $A_v = g_{m1}/G_o$ .

[4]

b.

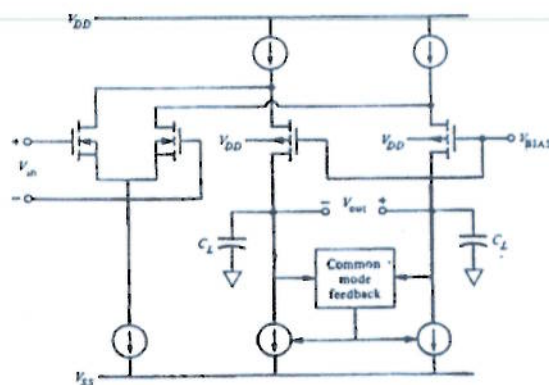

[6]

c)

Circuit is a differential continuous time integrator with a balanced double differential linear active transresistor.

$$I_1 = 2\beta[(V_g - V_x - V_T)(V_m/2 - V_x) - 1/2(V_m/2 - V_x)^2]$$

$$I_2 = 2\beta[(V_g - V_x - V_T)(-V_m/2 - V_x) - 1/2(-V_m/2 - V_x)^2]$$

$$R = 2V_m / (I_1 - I_2)$$

$$R = \frac{1}{\beta(V_g - V_T)}$$

[5]


Time constant  $\tau = RC = 10\text{ms}$   
 $R = 1/20 \times 5(1-0.5) = 20\text{ K}\Omega$   
 $C = \tau/R = 10\text{m}/20\text{K} = 5 \times 10^{-7}\text{ f}$

[5]

Answers to question 5:

5.a) Explain sigma delta operation (bookwork).

[5]

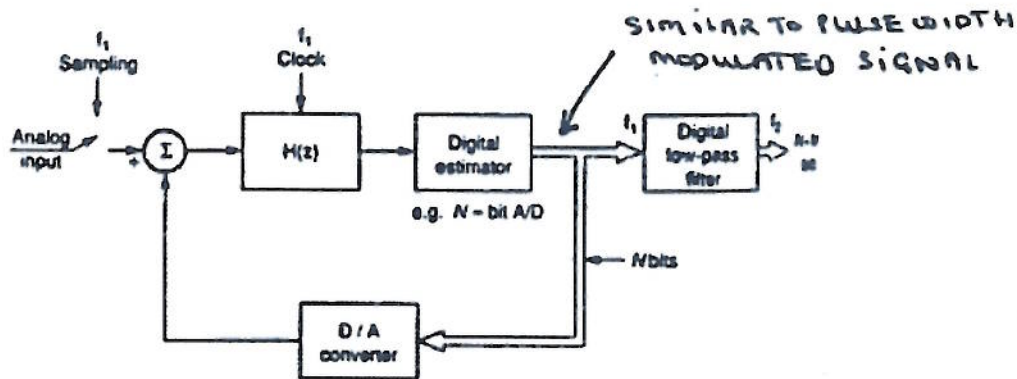


*Typical oversampled  $\Sigma$ - $\Delta$  (modulator) converter architecture .*

[5]

b)(i) Explain how the conversion works (bookwork)

[3]

Draw a cascade of blocks whereby  $N=8$

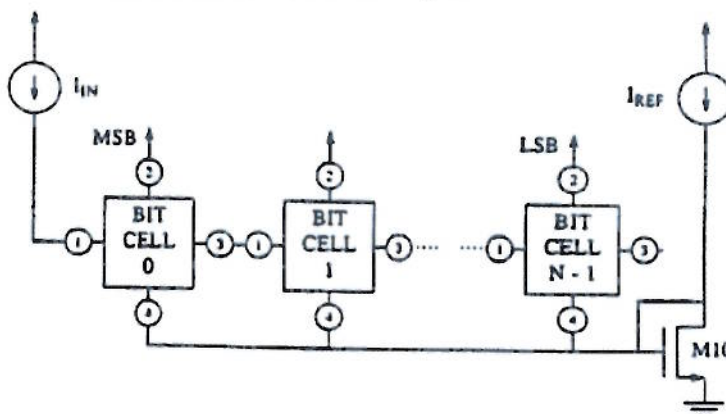

[4]

c)  $kT/C$  noise limits the resolution of a sampled data converter.


$$DR = 2^N = V_{ref}/\text{Noise} = V_{ref} / \sqrt{(kT \cdot 10Rf_c)}$$

[3]



Answers to question 6:

 6.a. 3rd-order Chebyshev low pass switched-capacitor ladder filter.



[5]


b. General transformation rules for ladder prototypes:

$$\text{Inductor: } \frac{f_c L_2}{R_s} = \frac{C_{L2}}{C_u}$$

$$\text{Capacitor: } \frac{C_{c3}}{C_u} = f_c R_s C_3$$

Resistor \$R\_s\$=dummy scalar.

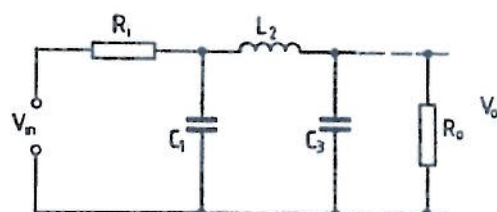The circuit is equivalent to an RLC prototype



[5]

c. For switched capacitor equivalent:

$$C_{c1}=C_{c3}=5.08 \text{ pF}$$

$$C_{L2}=3.49 \text{ pF.}$$

$$C_u=1 \text{ pF}$$

Assume scaling \$R\_s=R\_i=R\_o=1\Omega\$

Therefore

$$L_2 = C_{L2}/f_c = 3.49/100 \times 10^3 = 3.49 \times 10^{-5} \text{ H}$$

Normalised 1rad/sec we multiply by \$2\pi f\_0\$

$$L_2 = 3.49 \times 10^{-5} \times 2\pi \times 5 \text{ KHz} = 1.096 \text{ H}$$

$$C_1=C_3=C_{c3}/f_c = 5.08/100 \times 10^3 = 5.08 \times 10^{-5} \text{ f}$$

Normalised value \$C\_1=C\_3=1.596\$